

Specifications:-

(i) atleast 40dB (let's take 60dB) of DC gain.

(ii). GBW = 5MHz

(iii) PM $\geq 60^\circ$

(iv) Slew rate $\geq 10V/\mu\text{sec}$

(v) $I_{CMR}(+) = 1.6V$ $I_{CMR}(-) = 0.8V$

(vi) let's take $C_L = 10pF$

(vii) $V_{DD} = 1.8V$.

(viii) $\mu_{n\text{ox}} = 200 \mu A/V^2$ (initially)

$\mu_{p\text{ox}} = 100 \mu A/V^2$ (initial)

Calculations:-

$$\text{Slew rate} = \frac{I_T}{C_C}$$

and for $\geq 60^\circ$ phase margin

$$C_C = 0.4 C_L = 4pF.$$

$$I_T \geq 10 \times 10^{-6} \times 4 \times 10^{-12}$$

$$I_{D7} \approx 40 \mu A$$

M_1 & M_2

$$g_{m1} = GBW \cdot C_c \cdot 2\pi$$

$$g_{m1} = 5 \times 10^6 \times 2\pi \times 4 \times 10^{-12}$$

$$g_{m1} \rightarrow 40\pi \mu S$$

$$g_{m1} = 125 \mu S$$

$$g_{m1} = \sqrt{I_{D7} \mu_n C_{ox} \left(\frac{W}{L}\right)}$$

$$\Rightarrow \left(\frac{W}{L}\right)_1 = \frac{g_{m1}^2}{\mu_n C_{ox} I_{D7}} = \frac{(125)^2}{230 \times 40} = 1.69$$

from the Rough slide we get

$$\left(\frac{W}{L}\right)_2 = 1.69$$

$$\sqrt{\frac{P_{DS}}{B_3}} = V_{DD} - |V_{th3}| + V_{th1} - V_{in})_{max}$$

$$\left(\frac{W}{L}\right)_{3,4} = \frac{I_S}{\mu_{pcox} (V_{DD} - |V_{th3}| + V_{th1} - V_{inmax})^2}$$

$$\left(\frac{W}{L}\right)_{3,4} = \frac{40 \mu A}{100 \frac{\mu A}{V^2} (1.8 - 0.37 + 0.31 - 1.6)^2}$$

$$\left(\frac{W}{L}\right)_{3,4} = 20 \times 40$$

Since $I_{I7} \geq 40 \mu A$ and $I_{ref} = 4 \mu A$

So, 10 times current

So, factor is ≥ 10 Assume

$\left(\frac{W}{L}\right)_{M0} = 2$, then we must

have $\left(\frac{W}{L}\right)_{7,8} \geq 2 \times 10 = 20$.

I took it to be 40 for good gain.

for reasonable phase margin ($\sim 60^\circ$)

$$gm_5 = 2.2 gm_4 \left(\frac{C_L}{C_C} \right) !!$$

$$\downarrow gm_5 \gg 10 gm_1.$$

$$\Rightarrow V_{SG_4} = V_{SG_5} = 5$$

$$\hookrightarrow \left(\frac{W}{L} \right)_5 = \left(\frac{W}{L} \right)_4 \left(\frac{gm_5}{gm_4} \right)$$

$$\left(P_2 = \frac{gm_5}{2\pi C_L} \right) !! \quad (\text{corner purely from the Second Stage}).$$

$$GBW = 5 \text{ MHz}$$

$$P_2 \geq 2.2 \times 5 \text{ MHz} = 11 \text{ MHz}$$

$$P_2 \approx \frac{gm_5}{2\pi C_L}$$

$$11 \times 10^6 = \frac{gm_5}{2\pi \times (10 \times 10^{-6})}$$

$$gm_5 \geq 691 \mu\text{S}$$

now Since overdrive in both are same:-

$(V_{SG2} - |V_{TP}|)$ is same both M_4 and M_5 ;

$$\begin{aligned} g_{m4} &= \sqrt{2\mu_p C_{ox} (W/L)_4 I_{D4}} \\ &= \sqrt{2 \times 100/\mu \times 20.45 (20) \mu A} \\ &= 286 \mu S \end{aligned}$$

$$\begin{aligned} \Delta V_{O4} &= \frac{2 I_{D4}}{g_{m4}} = \frac{2 (20 \mu A)}{286 \mu S} \\ &= 0.14 V \end{aligned}$$

So for better phase margin we already got

$$g_{m5} \geq 691 \mu S$$

we must have $\Delta V_S = \Delta V_D = 0.14 V$

$$g_{m5} = \frac{2 I_{D5}}{V_{OV5}}$$

$$I_{D5} = \frac{691 \mu S \times 0.14}{2} = 48.37 \mu A$$

lets assume ($\approx 55 \mu A$)

$$(W/L)_5 = 20.45 \times 2.75 = 56.2375.$$

$$W = 25.551 \mu m, L = 0.15 \mu m$$

now

M_6 must be able to pull this much current

$$\left(\frac{S_S}{Q}\right) = \text{multiplier}$$

$$\frac{S_S}{Q} \times 1.69 \approx \frac{S_S}{Q} \times 2 = 27.5$$

$$\text{So, } \left(\frac{W}{L}\right)_6 = 27.5$$

Now we see what we get from the LtSpice:-

(i) dc gain: 64.783 dB (≥ 60 dB).

(ii) Phase margin at 0dB = 65°

(iii). GBW ≈ 4.7 MHz.

(iv) Currents in each transistor:-

$$M_0 = 4 \mu A$$

$$M_1 = 27.87 \mu A$$

$$M_2 = 27.74 \mu A$$

$$M_3 = 27.87 \mu A$$

← All of these are dc currents.

(This is little small due to the fact that it single handedly

$$M_4 = 27.74 \mu A$$

$$M_7 = 55.62 \mu A$$

$$M_5 = 46.8984 \mu A$$

$$M_6 = 46.8984 \mu A$$

justifies the saturation of
the M_5, M_6 transistor for
maximum gain

$$\left(\frac{W}{L}\right)_0 = 2 ; \quad \left(\frac{W}{L}\right)_7 = 40 \quad \left(\frac{W}{L}\right)_{1,2} = 1.69$$

$$\left(\frac{W}{L}\right)_{3,4} = 20.45 \quad \left(\frac{W}{L}\right)_5 = 51.1 \quad \left(\frac{W}{L}\right)_6 = 25.5$$

now ; if we calculate the g_m and the r_o

we have $r_o = \frac{1}{\lambda I_D}$ &

$$g_m = \sqrt{2 \mu_n C_{ox} \left(\frac{W}{L}\right) \cdot I_D}$$

μA

Tr No.	$r_o (K\Omega)$	$g_m (\mu S)$	$\Delta V (V)$	W/L	I_D
M_0	2500	60.7	0.132	2.0	4.0
M_1	360	147	0.378	1.69	27.8
M_2	360	147	0.378	1.69	27.8
M_3	360	337.2	0.165	20.45	27.8
M_4	360	337.2	0.165	20.45	27.8
M_5	180	1011.6	0.110	40	46.9
M_6	213	692.3	0.135	51.1	46.9
M_7	213	734.4	0.128	25.5	55.5



T ₀	W	L
M ₀	1.0 μm	0.5 μm
M ₁	0.855 μm	0.5 μm
M ₂	0.855 μm	0.5 μm
M ₃	10.22 μm	0.5 μm
M ₄	10.22 μm	0.5 μm
M ₅	25.55 μm	0.5 μm

everything
in μm .


M ₆	12.5 μm	0.5 μm
M ₇	20 μm	0.5 μm

Diagrams and Simulations:-

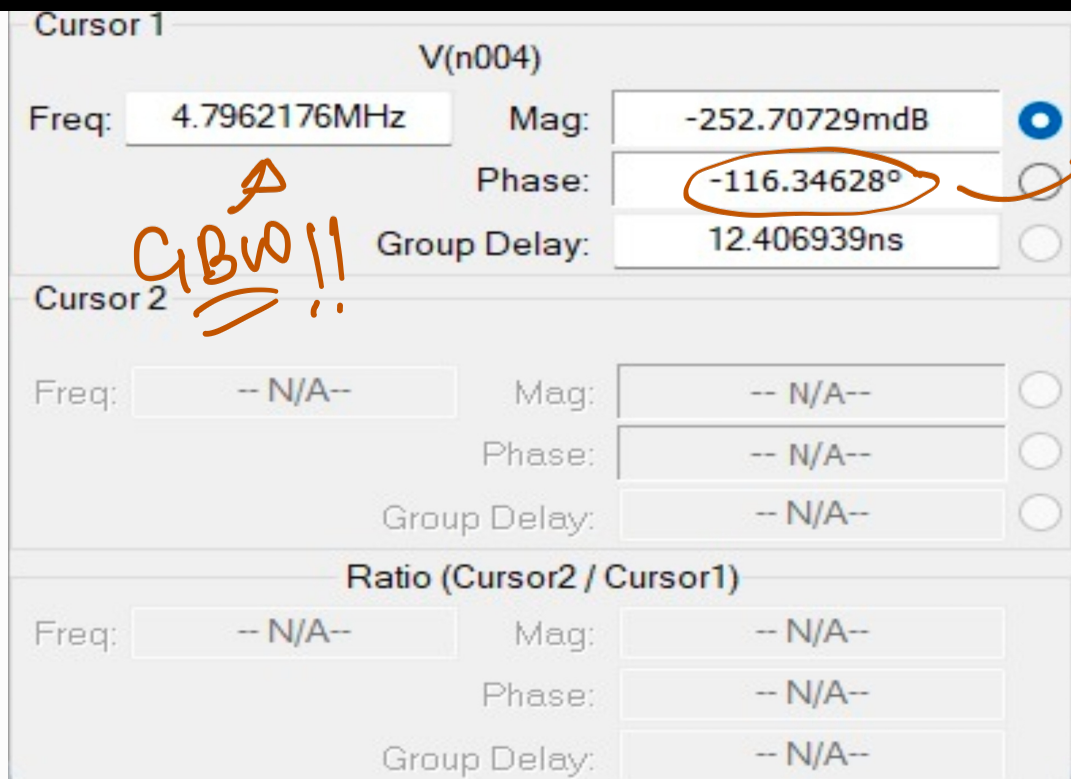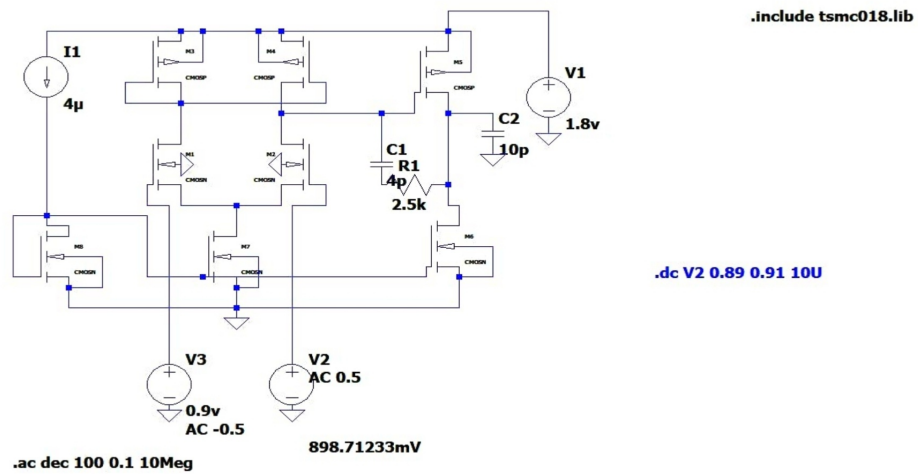Final circuit :- open loop
characteristics:-



Closed loop :-

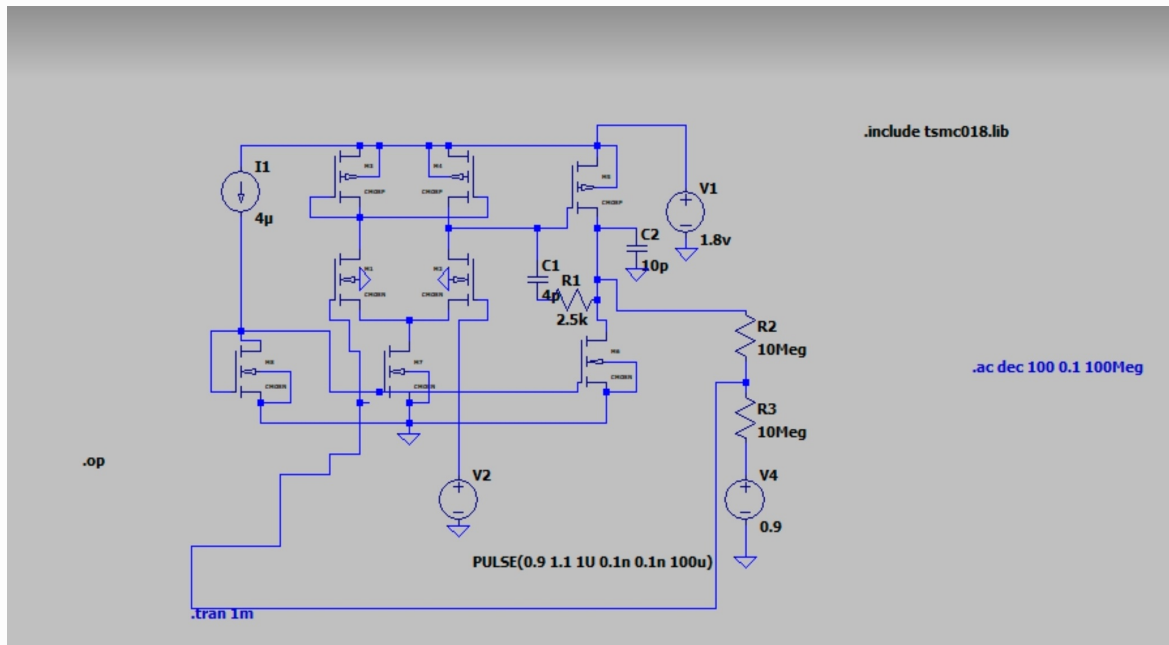

Transient response:-



operating points:-

```
V(n001):      1.8      voltage
V(n002):      1.15744  voltage
V(n003):      1.19874  voltage
V(n004):      0.902604  voltage
V(n005):      0.9      voltage
V(n006):      0.902604  voltage
V(n007):      0.901302  voltage
V(n008):      0.0849597 voltage
V(n009):      0.557781  voltage
V(n010):      0.9      voltage
I(C1):        1.18453e-24 device_current
I(C2):        9.02604e-24 device_current
I(I1):        4e-06      device_current
I(R1):        0          device_current
I(R2):        1.30188e-10 device_current
I(R3):        1.30188e-10 device_current
I(V1):        -0.000106646 device_current
I(V2):        0          device_current
I(V4):        1.30188e-10 device_current
Ib(M1):       -1.26203e-12 device_current
Ib(M2):       -1.30332e-12 device_current
Ib(M3):       6.52559e-13  device_current
Ib(M4):       6.11263e-13  device_current
Ib(M5):       9.07396e-13  device_current
Ib(M6):       -9.12604e-13 device_current
Ib(M7):       -9.45853e-14 device_current
Ib(M8):       -5.67781e-13 device_current
```

```
Ib(M8):       -5.67781e-13 device_current
Id(M1):       2.79511e-05  device_current
Id(M2):       2.78263e-05  device_current
Id(M3):       2.79511e-05  device_current
Id(M4):       2.78263e-05  device_current
Id(M5):       4.68687e-05  device_current
Id(M6):       4.68686e-05  device_current
Id(M7):       5.57773e-05  device_current
Id(M8):       4e-06        device_current
Ig(M1):       0            device_current
Ig(M2):       0            device_current
Ig(M3):       -0           device_current
Ig(M4):       -0           device_current
Ig(M5):       -0           device_current
Ig(M6):       0            device_current
Ig(M7):       0            device_current
Ig(M8):       0            device_current
Is(M1):       -2.79511e-05  device_current
Is(M2):       -2.78263e-05  device_current
Is(M3):       -2.79511e-05  device_current
Is(M4):       -2.78263e-05  device_current
Is(M5):       -4.68687e-05  device_current
Is(M6):       -4.68686e-05  device_current
Is(M7):       -5.57773e-05  device_current
Is(M8):       -4e-06        device_current
```